

## . 4 . *Fault Calculations*

Introduction	4.1
Three phase fault calculations	4.2
Symmetrical component analysis of a three-phase network	4.3
Equations and network connections for various types of faults	4.4
Current and voltage distribution in a system due to a fault	4.5
Effect of system earthing on zero sequence quantities	4.6
References	4.7

## • 4 • *Fault Calculations*

### 4.1 INTRODUCTION

A power system is normally treated as a balanced symmetrical three-phase network. When a fault occurs, the symmetry is normally upset, resulting in unbalanced currents and voltages appearing in the network. The only exception is the three-phase fault, which, because it involves all three phases equally at the same location, is described as a symmetrical fault. By using symmetrical component analysis and replacing the normal system sources by a source at the fault location, it is possible to analyse these fault conditions.

For the correct application of protection equipment, it is essential to know the fault current distribution throughout the system and the voltages in different parts of the system due to the fault. Further, boundary values of current at any relaying point must be known if the fault is to be cleared with discrimination. The information normally required for each kind of fault at each relaying point is:

- i. maximum fault current
- ii. minimum fault current
- iii. maximum through fault current

To obtain the above information, the limits of stable generation and possible operating conditions, including the method of system earthing, must be known. Faults are always assumed to be through zero fault impedance.

### 4.2 THREE-PHASE FAULT CALCULATIONS

Three-phase faults are unique in that they are balanced, that is, symmetrical in the three phases, and can be calculated from the single-phase impedance diagram and the operating conditions existing prior to the fault.

A fault condition is a sudden abnormal alteration to the normal circuit arrangement. The circuit quantities, current and voltage, will alter, and the circuit will pass through a transient state to a steady state. In the transient state, the initial magnitude of the fault current will depend upon the point on the voltage wave at which the fault occurs. The decay of the transient condition, until it merges into steady state, is a function of the parameters of the circuit elements. The transient current may be regarded as a d.c. exponential current

superimposed on the symmetrical steady state fault current. In a.c. machines, owing to armature reaction, the machine reactances pass through 'sub transient' and 'transient' stages before reaching their steady state synchronous values. For this reason, the resultant fault current during the transient period, from fault inception to steady state also depends on the location of the fault in the network relative to that of the rotating plant.

In a system containing many voltage sources, or having a complex network arrangement, it is tedious to use the normal system voltage sources to evaluate the fault current in the faulty branch or to calculate the fault current distribution in the system. A more practical method [4.1] is to replace the system voltages by a single driving voltage at the fault point. This driving voltage is the voltage existing at the fault point before the fault occurs.

Consider the circuit given in Figure 4.1 where the driving voltages are  $\bar{E}$  and  $\bar{E}'$ , the impedances on either side of fault point  $F$  are  $\bar{Z}'_1$  and  $\bar{Z}''_1$ , and the current through point  $F$  before the fault occurs is  $\bar{I}$ .

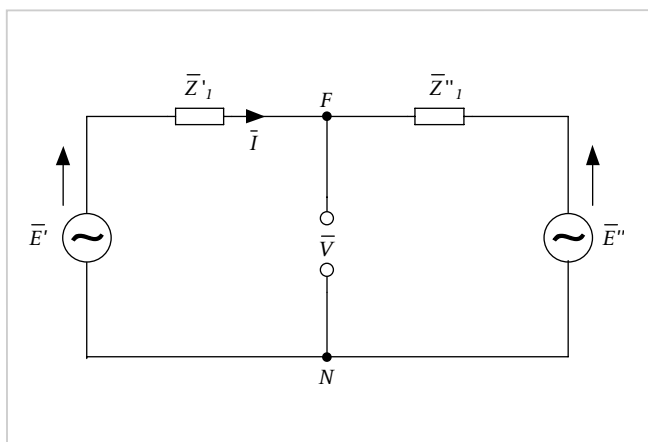


Figure 4.1: Network with fault at F

The voltage  $\bar{V}$  at  $F$  before fault inception is:

$$\bar{V} = \bar{E} - \bar{I} \bar{Z}'_1 = \bar{E}' + \bar{I} \bar{Z}''_1$$

After the fault the voltage  $\bar{V}$  is zero. Hence, the change in voltage is  $-\bar{V}$ . Because of the fault, the change in the current flowing into the network from  $F$  is:

$$\Delta \bar{I} = -\frac{\bar{V}}{\bar{Z}_1} = -\bar{V} \frac{(\bar{Z}'_1 + \bar{Z}''_1)}{\bar{Z}'_1 \bar{Z}''_1}$$

and, since no current was flowing into the network from  $F$  prior to the fault, the fault current flowing from the network into the fault is:

$$\bar{I}_f = -\Delta \bar{I} = \bar{V} \frac{(\bar{Z}'_1 + \bar{Z}''_1)}{\bar{Z}'_1 \bar{Z}''_1}$$

By applying the principle of superposition, the load currents circulating in the system prior to the fault may

be added to the currents circulating in the system due to the fault, to give the total current in any branch of the system at the time of fault inception. However, in most problems, the load current is small in comparison to the fault current and is usually ignored.

In a practical power system, the system regulation is such that the load voltage at any point in the system is within 10% of the declared open-circuit voltage at that point. For this reason, it is usual to regard the pre-fault voltage at the fault as being the open-circuit voltage, and this assumption is also made in a number of the standards dealing with fault level calculations.

For an example of practical three-phase fault calculations, consider a fault at  $A$  in Figure 3.9. With the network reduced as shown in Figure 4.2, the load voltage at  $A$  before the fault occurs is:

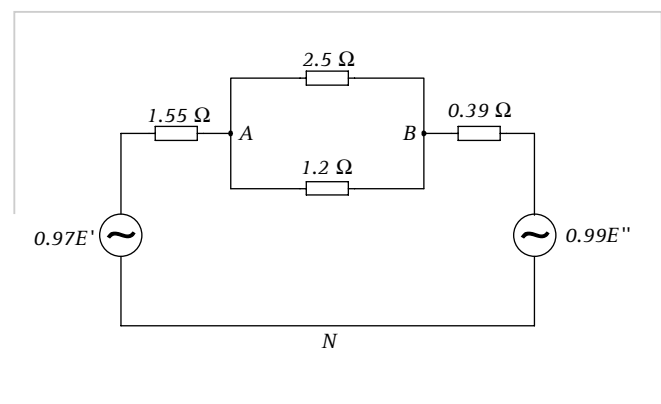


Figure 4.2: Reduction of typical power system network

$$\bar{V} = 0.97 \bar{E}' - 1.55 \bar{I}$$

$$\bar{V} = 0.99 \bar{E}'' + \left( \frac{1.2 \times 2.5}{2.5 + 1.2} + 0.39 \right) \bar{I}$$

For practical working conditions,  $\bar{E}' \gg 1.55 \bar{I}$  and  $\bar{E}'' \gg 1.207 \bar{I}$ . Hence  $\bar{E}' \cong \bar{E}'' \cong \bar{V}$ .

Replacing the driving voltages  $\bar{E}'$  and  $\bar{E}''$  by the load voltage  $\bar{V}$  between  $A$  and  $N$  modifies the circuit as shown in Figure 4.3(a).

The node  $A$  is the junction of three branches. In practice, the node would be a busbar, and the branches are feeders radiating from the bus via circuit breakers, as shown in Figure 4.3(b). There are two possible locations for a fault at  $A$ ; the busbar side of the breakers or the line side of the breakers. In this example, it is assumed that the fault is at  $X$ , and it is required to calculate the current flowing from the bus to  $X$ .

The network viewed from  $AN$  has a driving point impedance  $|Z_1| = 0.68 \text{ ohms}$ .

The current in the fault is  $\left| \frac{V}{Z_1} \right|$ .

Let this current be 1.0 per unit. It is now necessary to find the fault current distribution in the various branches of the network and in particular the current flowing from A to X on the assumption that a relay at X is to detect the fault condition. The equivalent impedances viewed from either side of the fault are shown in Figure 4.4(a).

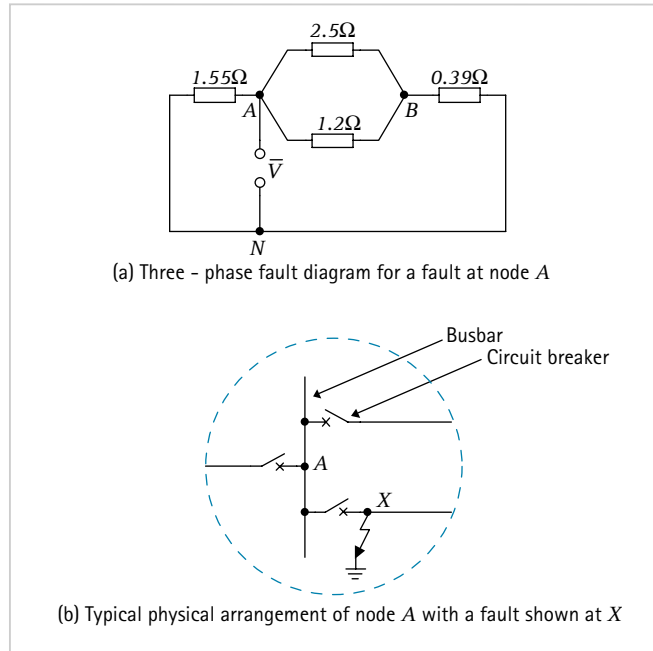


Figure 4.3: Network with fault at node A

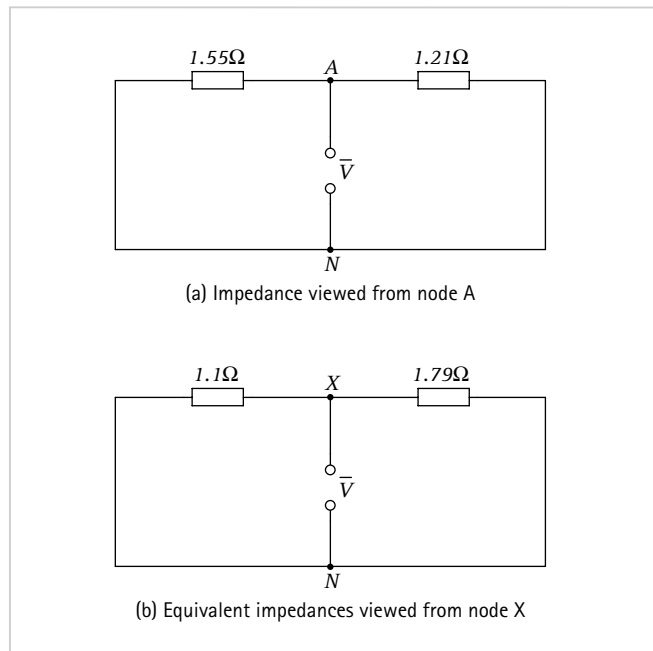


Figure 4.4: Impedances viewed from fault

The currents from Figure 4.4(a) are as follows:

$$\text{From the right: } \frac{1.55}{2.76} = 0.563 \text{ p.u.}$$

$$\text{From the left: } \frac{1.21}{2.76} = 0.437 \text{ p.u.}$$

There is a parallel branch to the right of A

Therefore, current in 2.5 ohm branch

$$= \frac{1.2 \times 0.563}{3.7} = 0.183 \text{ p.u.}$$

and the current in 1.2 ohm branch

$$= \frac{2.5 \times 0.563}{3.7} = 0.38 \text{ p.u.}$$

Total current entering X from the left, that is, from A to X, is  $0.437 + 0.183 = 0.62 \text{ p.u.}$  and from B to X is  $0.38 \text{ p.u.}$  The equivalent network as viewed from the relay is as shown in Figure 4.4(b). The impedances on either side are:

$$0.68/0.62 = 1.1 \text{ ohms}$$

and

$$0.68/0.38 = 1.79 \text{ ohms}$$


The circuit of Figure 4.4 (b) has been included because the Protection Engineer is interested in these equivalent parameters when applying certain types of protection relay.

#### 4.3 SYMMETRICAL COMPONENT ANALYSIS OF A THREE-PHASE NETWORK

The Protection Engineer is interested in a wider variety of faults than just a three-phase fault. The most common fault is a single-phase to earth fault, which, in LV systems, can produce a higher fault current than a three-phase fault. Similarly, because protection is expected to operate correctly for all types of fault, it may be necessary to consider the fault currents due to many different types of fault. Since the three-phase fault is unique in being a balanced fault, a method of analysis that is applicable to unbalanced faults is required. It can be shown [4.2] that, by applying the 'Principle of Superposition', any general three-phase system of vectors may be replaced by three sets of balanced (symmetrical) vectors; two sets are three-phase but having opposite phase rotation and one set is co-phasal. These vector sets are described as the positive, negative and zero sequence sets respectively.

The equations between phase and sequence voltages are given below:
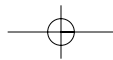
$$\left. \begin{aligned} \bar{E}_a &= \bar{E}_1 + \bar{E}_2 + \bar{E}_0 \\ \bar{E}_b &= a^2 \bar{E}_1 + a \bar{E}_2 + \bar{E}_0 \\ \bar{E}_c &= a \bar{E}_1 + a^2 \bar{E}_2 + \bar{E}_0 \end{aligned} \right\} \dots \text{Equation 4.1}$$



$$\left. \begin{aligned} \bar{E}_1 &= \frac{1}{3}(\bar{E}_a + a\bar{E}_b + a^2\bar{E}_c) \\ \bar{E}_2 &= \frac{1}{3}(\bar{E}_a + a^2\bar{E}_b + a\bar{E}_c) \\ \bar{E}_0 &= \frac{1}{3}(\bar{E}_a + \bar{E}_b + \bar{E}_c) \end{aligned} \right\} \dots\text{Equation 4.2}$$

where all quantities are referred to the reference phase A. A similar set of equations can be written for phase and sequence currents. Figure 4.5 illustrates the resolution of a system of unbalanced vectors.

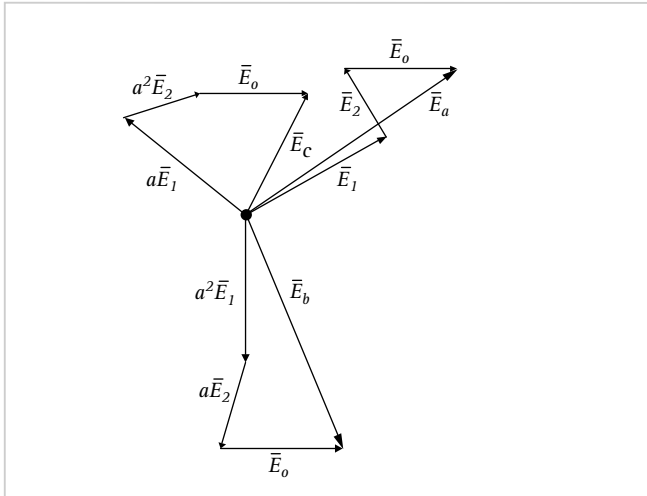


Figure 4.5: Resolution of a system of unbalanced vectors

When a fault occurs in a power system, the phase impedances are no longer identical (except in the case of three-phase faults) and the resulting currents and voltages are unbalanced, the point of greatest unbalance being at the fault point. It has been shown in Chapter 3 that the fault may be studied by short-circuiting all normal driving voltages in the system and replacing the fault connection by a source whose driving voltage is equal to the pre-fault voltage at the fault point. Hence, the system impedances remain symmetrical, viewed from the fault, and the fault point may now be regarded as the point of injection of unbalanced voltages and currents into the system.

This is a most important approach in defining the fault conditions since it allows the system to be represented by sequence networks [4.3] using the method of symmetrical components.

### 4.3.1 Positive Sequence Network

During normal balanced system conditions, only positive sequence currents and voltages can exist in the system, and therefore the normal system impedance network is a positive sequence network.

When a fault occurs in a power system, the current in the

fault branch changes from 0 to  $\bar{I}$  and the positive sequence voltage across the branch changes from  $\bar{V}$  to  $\bar{V}_1$ ; replacing the fault branch by a source equal to the change in voltage and short-circuiting all normal driving voltages in the system results in a current  $\Delta\bar{I}$  flowing into the system, and:

$$\Delta\bar{I} = -\frac{(\bar{V} - \bar{V}_1)}{\bar{Z}_1} \dots\text{Equation 4.3}$$

where  $\bar{Z}_1$  is the positive sequence impedance of the system viewed from the fault. As before the fault no current was flowing from the fault into the system, it follows that  $\bar{I}_1$ , the fault current flowing from the system into the fault must equal  $-\Delta\bar{I}$ . Therefore:

$$\bar{V}_1 = \bar{V} - \bar{I}_1 \bar{Z}_1 \dots\text{Equation 4.4}$$

is the relationship between positive sequence currents and voltages in the fault branch during a fault.

In Figure 4.6, which represents a simple system, the voltage drops  $\bar{I}_1' \bar{Z}_1'$  and  $\bar{I}_1'' \bar{Z}_1''$  are equal to  $(\bar{V} - \bar{V}_1)$  where the currents  $\bar{I}_1'$  and  $\bar{I}_1''$  enter the fault from the left and right respectively and impedances  $\bar{Z}_1'$  and  $\bar{Z}_1''$  are the total system impedances viewed from either side of the fault branch. The voltage  $\bar{V}$  is equal to the open-circuit voltage in the system, and it has been shown that  $\bar{V} \cong \bar{E} \cong \bar{E}''$  (see Section 3.7). So the positive sequence voltages in the system due to the fault are greatest at the source, as shown in the gradient diagram, Figure 4.6(b).


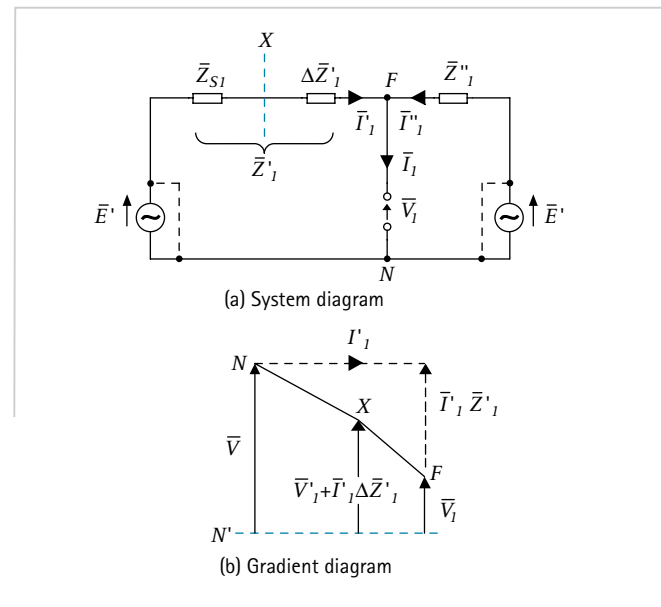


Figure 4.6: Fault at F: Positive sequence diagrams
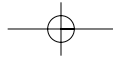
### 4.3.2 Negative Sequence Network

If only positive sequence quantities appear in a power system under normal conditions, then negative sequence quantities can only exist during an unbalanced fault.

If no negative sequence quantities are present in the



fault branch prior to the fault, then, when a fault occurs, the change in voltage is  $\bar{V}_2$ , and the resulting current  $\bar{I}_2$  flowing from the network into the fault is:

$$\bar{I}_2 = \frac{-\bar{V}_2}{\bar{Z}_2} \quad \dots \text{Equation 4.5}$$

The impedances in the negative sequence network are generally the same as those in the positive sequence network. In machines  $\bar{Z}_1 \neq \bar{Z}_2$ , but the difference is generally ignored, particularly in large networks.

The negative sequence diagrams, shown in Figure 4.7, are similar to the positive sequence diagrams, with two important differences; no driving voltages exist before the fault and the negative sequence voltage  $\bar{V}_2$  is greatest at the fault point.

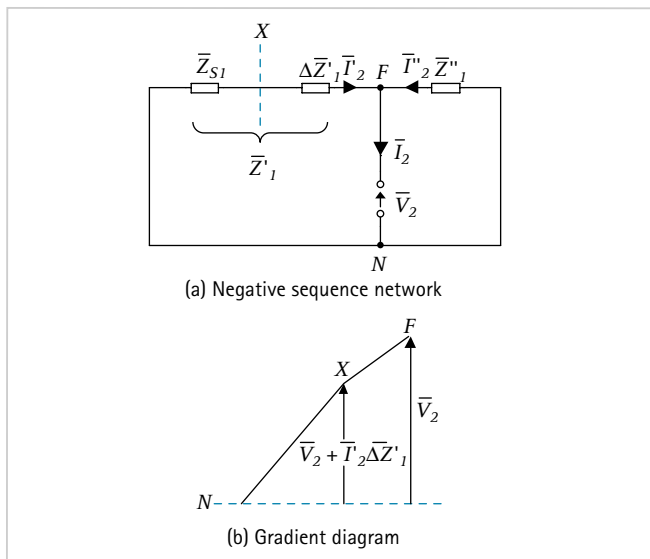


Figure 4.7: Fault at F: Negative sequence diagram

### 4.3.3 Zero Sequence Network

The zero sequence current and voltage relationships during a fault condition are the same as those in the negative sequence network. Hence:

$$\bar{V}_0 = -\bar{I}_0 \bar{Z}_0 \quad \dots \text{Equation 4.6}$$

Also, the zero sequence diagram is that of Figure 4.7, substituting  $\bar{I}_0$  for  $\bar{I}_2$ , and so on.

The currents and voltages in the zero sequence network are co-phasal, that is, all the same phase. For zero sequence currents to flow in a system there must be a return connection through either a neutral conductor or the general mass of earth. Note must be taken of this fact when determining zero sequence equivalent circuits. Further, in general  $\bar{Z}_1 \neq \bar{Z}_0$  and the value of  $\bar{Z}_0$  varies according to the type of plant, the winding arrangement and the method of earthing.

## 4.4 EQUATIONS AND NETWORK CONNECTIONS FOR VARIOUS TYPES OF FAULTS

The most important types of faults are as follows:

- a. single-phase to earth
- b. phase to phase
- c. phase-phase-earth
- d. three-phase (with or without earth)

The above faults are described as single shunt faults because they occur at one location and involve a connection between one phase and another or to earth.

In addition, the Protection Engineer often studies two other types of fault:

- e. single-phase open circuit
- f. cross-country fault

By determining the currents and voltages at the fault point, it is possible to define the fault and connect the sequence networks to represent the fault condition. From the initial equations and the network diagram, the nature of the fault currents and voltages in different branches of the system can be determined.

For shunt faults of zero impedance, and neglecting load current, the equations defining each fault (using phase-neutral values) can be written down as follows:

- a. Single-phase-earth (A-E)

$$\left. \begin{aligned} \bar{I}_b &= 0 \\ \bar{I}_c &= 0 \\ \bar{V}_a &= 0 \end{aligned} \right\} \quad \dots \text{Equation 4.7}$$

- b. Phase-phase (B-C)

$$\left. \begin{aligned} \bar{I}_a &= 0 \\ \bar{I}_b &= -\bar{I}_c \\ \bar{V}_b &= \bar{V}_c \end{aligned} \right\} \quad \dots \text{Equation 4.8}$$


- c. Phase-phase-earth (B-C-E)

$$\left. \begin{aligned} \bar{I}_a &= 0 \\ \bar{V}_b &= 0 \\ \bar{V}_c &= 0 \end{aligned} \right\} \quad \dots \text{Equation 4.9}$$

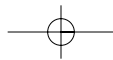- d. Three-phase (A-B-C or A-B-C-E)

$$\left. \begin{aligned} \bar{I}_a + \bar{I}_b + \bar{I}_c &= 0 \\ \bar{V}_a &= \bar{V}_b \\ \bar{V}_b &= \bar{V}_c \end{aligned} \right\} \quad \dots \text{Equation 4.10}$$

It should be noted from the above that for any type of fault there are three equations that define the fault conditions.



When there is a fault impedance, this must be taken into account when writing down the equations. For example, with a single-phase-earth fault through fault impedance  $\bar{Z}_f$ , Equations 4.7 are re-written:

$$\left. \begin{aligned} \bar{I}_b &= 0 \\ \bar{I}_c &= 0 \\ \bar{V}_a &= \bar{I}_a \bar{Z}_f \end{aligned} \right\} \dots \text{Equation 4.11}$$

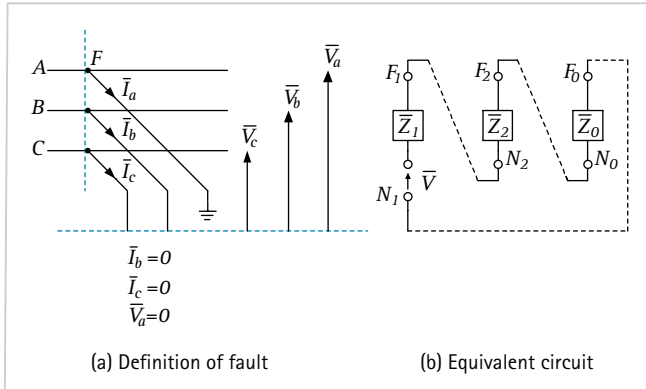


Figure 4.8: Single-phase-earth fault at F

#### 4.4.1 Single-phase-earth Fault (A-E)

Consider a fault defined by Equations 4.7 and by Figure 4.8(a). Converting Equations 4.7 into sequence quantities by using Equations 4.1 and 4.2, then:

$$\bar{I}_1 = \bar{I}_2 = \bar{I}_0 = \frac{1}{3} \bar{I}_a \dots \text{Equation 4.12}$$

$$\bar{V}_1 = -(\bar{V}_2 + \bar{V}_0) \dots \text{Equation 4.13}$$

Substituting for  $\bar{V}_1$ ,  $\bar{V}_2$  and  $\bar{V}_0$  in Equation 4.13 from Equations 4.4, 4.5 and 4.6:

$$\bar{V} - \bar{I}_1 \bar{Z}_1 = \bar{I}_2 \bar{Z}_2 + \bar{I}_0 \bar{Z}_0$$

but, from Equation 4.12,  $\bar{I}_1 = \bar{I}_2 = \bar{I}_0$ , therefore:

$$\bar{V} = \bar{I}_1 (\bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3) \dots \text{Equation 4.14}$$

The constraints imposed by Equations 4.12 and 4.14 indicate that the equivalent circuit for the fault is obtained by connecting the sequence networks in series, as shown in Figure 4.8(b).

#### 4.4.2 Phase-phase Fault (B-C)

From Equation 4.8 and using Equations 4.1 and 4.2:

$$\bar{I}_1 = -\bar{I}_2 \dots \text{Equation 4.15}$$

$$\bar{I}_0 = 0$$

$$\bar{V}_1 = \bar{V}_2 \dots \text{Equation 4.16}$$

From network Equations 4.4 and 4.5, Equation 4.16 can be re-written:

$$\bar{V} - \bar{I}_1 \bar{Z}_1 = \bar{I}_2 \bar{Z}_2 + \bar{I}_0 \bar{Z}_0$$

$$\bar{V} - \bar{I}_1 \bar{Z}_1 = \bar{I}_2 \bar{Z}_2$$

and substituting for  $\bar{I}_2$  from Equation 4.15:

$$\bar{V} = \bar{I}_1 (\bar{Z}_1 + \bar{Z}_2) \dots \text{Equation 4.17}$$

The constraints imposed by Equations 4.15 and 4.17 indicate that there is no zero sequence network connection in the equivalent circuit and that the positive and negative sequence networks are connected in parallel. Figure 4.9 shows the defining and equivalent circuits satisfying the above equations.

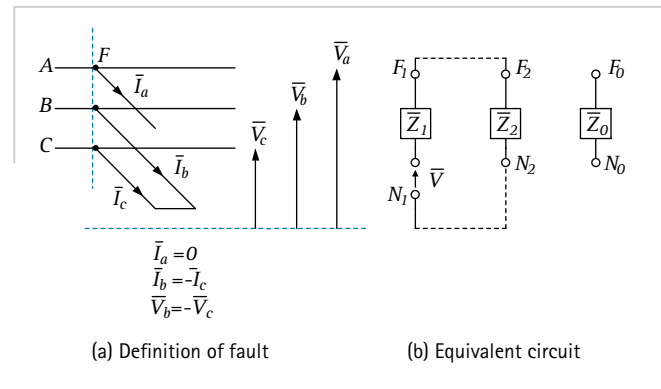


Figure 4.9: Phase-Phase fault at F

#### 4.4.3 Phase-phase-earth Fault (B-C-E)

Again, from Equation 4.9 and Equations 4.1 and 4.2:

$$\bar{I}_1 = -(\bar{I}_2 + \bar{I}_0) \dots \text{Equation 4.18}$$

and

$$\bar{V}_1 = \bar{V}_2 = \bar{V}_0 \dots \text{Equation 4.19}$$

Substituting for  $\bar{V}_2$  and  $\bar{V}_0$  using network Equations 4.5 and 4.6:

$$\bar{I}_2 \bar{Z}_2 = \bar{I}_0 \bar{Z}_0$$

thus, using Equation 4.18:

$$\bar{I}_0 = -\frac{\bar{Z}_2 \bar{I}_1}{\bar{Z}_0 + \bar{Z}_2} \dots \text{Equation 4.20}$$

$$\bar{I}_2 = -\frac{\bar{Z}_0 \bar{I}_1}{\bar{Z}_0 + \bar{Z}_2} \dots \text{Equation 4.21}$$

Now equating  $\bar{V}_1$  and  $\bar{V}_2$  and using Equation 4.4 gives:

$$\bar{V} - \bar{I}_1 \bar{Z}_1 = -\bar{I}_2 \bar{Z}_2$$

or


$$\bar{V} = \bar{I}_1 \bar{Z}_1 - \bar{I}_2 \bar{Z}_2$$

Substituting for  $\bar{I}_2$  from Equation 4.21:

$$\bar{V} = \left[ \bar{Z}_1 + \frac{\bar{Z}_0 \bar{Z}_2}{\bar{Z}_0 + \bar{Z}_2} \right] \bar{I}_1$$

or
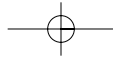
$$\bar{I}_1 = \bar{V} \frac{(\bar{Z}_0 + \bar{Z}_2)}{\bar{Z}_1 \bar{Z}_0 + \bar{Z}_1 \bar{Z}_2 + \bar{Z}_0 \bar{Z}_2} \dots \text{Equation 4.22}$$



From the above equations it follows that connecting the three sequence networks in parallel as shown in Figure 4.10(b) may represent a phase-phase-earth fault.

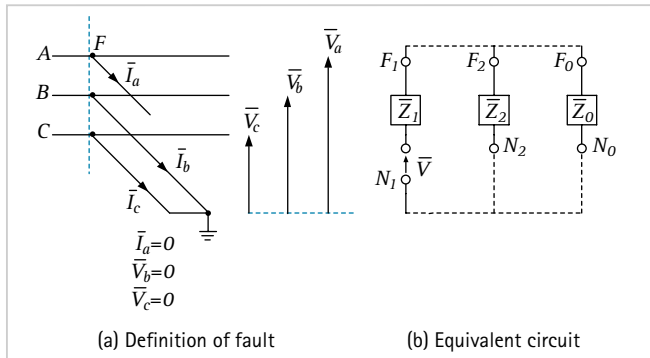


Figure 4.10: Phase-phase-earth fault at F

#### 4.4.4 Three-phase Fault (A-B-C or A-B-C-E)

Assuming that the fault includes earth, then, from Equations 4.10 and 4.1, 4.2, it follows that:

$$\left. \begin{aligned} \bar{V}_0 &= \bar{V}_a \\ \bar{V}_1 &= \bar{V}_2 = 0 \end{aligned} \right\} \dots\text{Equation 4.23}$$

and

$$\bar{I}_0 = 0 \dots\text{Equation 4.24}$$

Substituting  $\bar{V}_2 = 0$  in Equation 4.5 gives:

$$\bar{I}_2 = 0 \dots\text{Equation 4.25}$$

and substituting  $\bar{V}_1 = 0$  in Equation 4.4:

$$0 = \bar{V}_1 - \bar{I}_1 \bar{Z}_1$$

or

$$\bar{V} = \bar{I}_1 \bar{Z}_1 \dots\text{Equation 4.26}$$

Further, since from Equation 4.24  $\bar{I}_0 = 0$ , it follows from Equation 4.6 that  $\bar{V}_0$  is zero when  $\bar{Z}_0$  is finite. The equivalent sequence connections for a three-phase fault are shown in Figure 4.11.

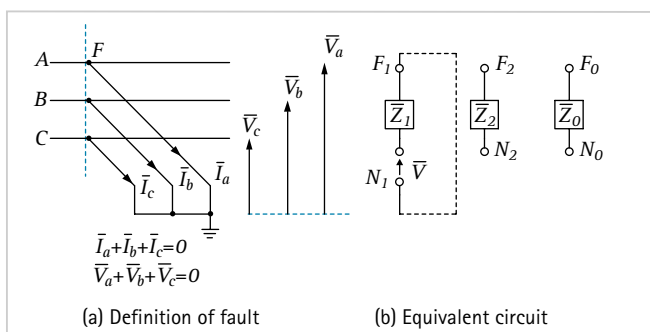


Figure 4.11: Three-phase-earth fault at F

#### 4.4.5 Single-phase Open Circuit Fault

The single-phase open circuit fault is shown diagrammatically in Figure 4.12(a). At the fault point, the boundary conditions are:

$$\left. \begin{aligned} I_a &= 0 \\ V_b = V_c &= 0 \end{aligned} \right\} \dots\text{Equation 4.27}$$

Hence, from Equations 4.2,

$$V_0 = 1/3 V_a$$

$$V_1 = 1/3 V_a$$

$$V_2 = 1/3 V_a$$

and therefore:

$$\left. \begin{aligned} V_1 = V_2 = V_0 &= 1/3 V_a \\ I_a = I_1 + I_2 + I_0 &= 0 \end{aligned} \right\} \dots\text{Equation 4.28}$$

From Equations 4.28, it can be concluded that the sequence networks are connected in parallel, as shown in Figure 4.12(b).

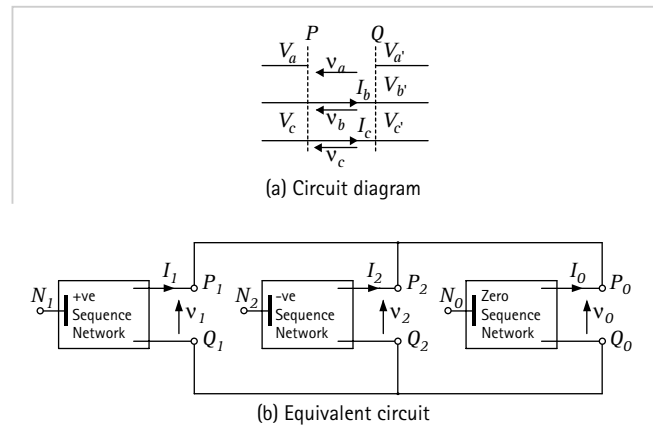


Figure 4.12: Open circuit on phase A

#### 4.4.6 Cross-country Faults

A cross-country fault is one where there are two faults affecting the same circuit, but in different locations and possibly involving different phases. Figure 4.13(a) illustrates this.

The constraints expressed in terms of sequence quantities are as follows:

a) At point F

$$\left. \begin{aligned} I_b + I_c &= 0 \\ V_a &= 0 \end{aligned} \right\} \dots\text{Equation 4.29}$$

Therefore:

$$\left. \begin{aligned} I_{a1} = I_{a2} = I_{a0} \\ V_{a1} + V_{a2} + V_{a0} &= 0 \end{aligned} \right\} \dots\text{Equation 4.30}$$

b) At point F'



$$\left. \begin{aligned} I'_a = I'_c &= 0 \\ V'_b &= 0 \end{aligned} \right\} \dots\text{Equation 4.31}$$

and therefore:


$$I'_{b1} = I'_{b2} = I'_{b0} \dots\text{Equation 4.32}$$

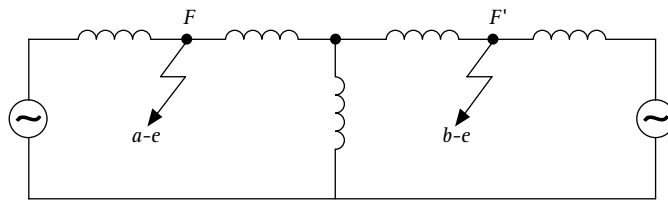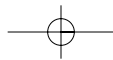To solve, it is necessary to convert the currents and voltages at point F' to the sequence currents in the same phase as those at point F. From Equation 4.32,





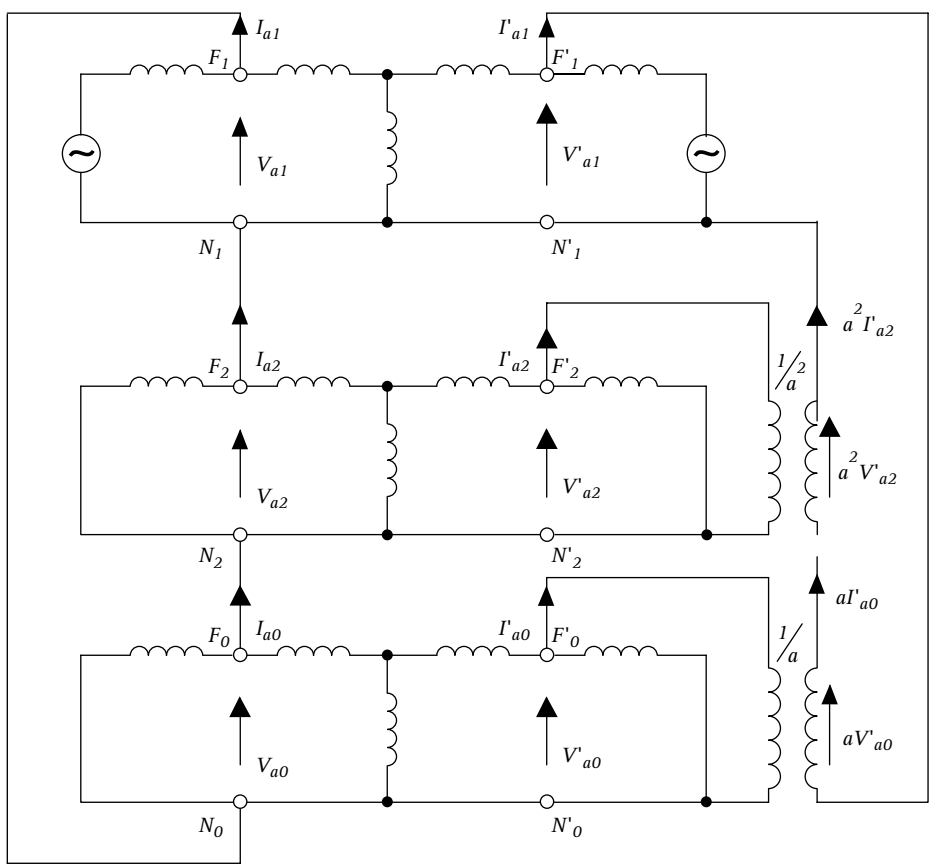(a) 'A' phase to ground at F and 'B' phase to ground at F'



(b) Equivalent circuit

Figure 4.13: Cross - country fault - phase A to phase B

Fault Calculations

• 4 •

$$a^2 I'_{a1} = a I'_{a2} = I'_{a0}$$

or

$$I'_{a1} = a^2 I'_{a2} = a I'_{a0} \quad \dots \text{Equation 4.33}$$

and, for the voltages

$$V'_{b1} + V'_{b2} + V'_{b0} = 0$$

Converting:

$$a^2 V'_{a1} + a V'_{a2} + V'_{a0} = 0$$

or


$$V'_{a1} + a^2 V'_{a2} + a V'_{a0} = 0 \quad \dots \text{Equation 4.34}$$

The fault constraints involve phase shifted sequence quantities. To construct the appropriate sequence networks, it is necessary to introduce phase-shifting transformers to couple the sequence networks. This is shown in Figure 4.13(b).
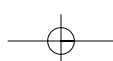
#### 4.5 CURRENT AND VOLTAGE DISTRIBUTION IN A SYSTEM DUE TO A FAULT

Practical fault calculations involve the examination of the effect of a fault in branches of network other than the faulted branch, so that protection can be applied correctly to isolate the section of the system directly involved in the fault. It is therefore not enough to calculate the fault current in the fault itself; the fault current distribution must also be established. Further, abnormal voltage stresses may appear in a system because of a fault, and these may affect the operation of the protection. Knowledge of current and voltage distribution in a network due to a fault is essential for the application of protection.

The approach to network fault studies for assessing the application of protection equipment may be summarised as follows:



- a. from the network diagram and accompanying data, assess the limits of stable generation and possible operating conditions for the system

**NOTE:** When full information is not available assumptions may have to be made

- b. with faults assumed to occur at each relaying point in turn, maximum and minimum fault currents are calculated for each type of fault

**NOTE:** The fault is assumed to be through zero impedance

- c. by calculating the current distribution in the network for faults applied at different points in the network (from (b) above) the maximum through fault currents at each relaying point are established for each type of fault

- d. at this stage more or less definite ideas on the type of protection to be applied are formed. Further calculations for establishing voltage variation at the relaying point, or the stability limit of the system with a fault on it, are now carried out in order to determine the class of protection necessary, such as high or low speed, unit or non-unit, etc.

### 4.5.1 Current Distribution

The phase current in any branch of a network is determined from the sequence current distribution in the equivalent circuit of the fault. The sequence currents are expressed in per unit terms of the sequence current in the fault branch.

In power system calculations, the positive and negative sequence impedances are normally equal. Thus, the division of sequence currents in the two networks will also be identical.

The impedance values and configuration of the zero sequence network are usually different from those of the positive and negative sequence networks, so the zero sequence current distribution is calculated separately.

If  $C_0$  and  $C_1$  are described as the zero and positive sequence distribution factors then the actual current in a sequence branch is given by multiplying the actual current in the sequence fault branch by the appropriate distribution factor. For this reason, if  $\bar{I}_1$ ,  $\bar{I}_2$  and  $\bar{I}_0$  are sequence currents in an arbitrary branch of a network due to a fault at some point in the network, then the phase currents in that branch may be expressed in terms of the distribution constants and the sequence currents in the fault. These are given below for the various common shunt faults, using Equation 4.1 and the appropriate fault equations:

- a. single-phase-earth (A-E)

$$\left. \begin{aligned} \bar{I}'_a &= (2C_1 + C_0)\bar{I}_0 \\ \bar{I}'_b &= -(C_1 - C_0)\bar{I}_0 \\ \bar{I}'_c &= -(C_1 - C_0)\bar{I}_0 \end{aligned} \right\}$$

...Equation 4.35

- b. phase-phase (B-C)

$$\left. \begin{aligned} \bar{I}'_a &= 0 \\ \bar{I}'_b &= (a^2 - a) C_1 \bar{I}_1 \\ \bar{I}'_c &= (a - a^2) C_1 \bar{I}_1 \end{aligned} \right\}$$

...Equation 4.36

- c. phase-phase-earth (B-C-E)

$$\left. \begin{aligned} \bar{I}'_a &= -(C_1 - C_0)\bar{I}_0 \\ \bar{I}'_b &= \left[ (a - a^2)C_1 \frac{\bar{Z}_0}{\bar{Z}_1} - a^2C_1 - C_0 \right] \bar{I}_0 \\ \bar{I}'_c &= \left[ (a^2 - a)C_1 \frac{\bar{Z}_0}{\bar{Z}_1} - aC_1 + C_0 \right] \bar{I}_0 \end{aligned} \right\}$$

...Equation 4.37

- d. three-phase (A-B-C or A-B-C-E)

$$\left. \begin{aligned} \bar{I}'_a &= C_1 \bar{I}_1 \\ \bar{I}'_b &= a^2 C_1 \bar{I}_1 \\ \bar{I}'_c &= a C_1 \bar{I}_1 \end{aligned} \right\}$$

...Equation 4.38

As an example of current distribution technique, consider the system in Figure 4.14(a). The equivalent sequence networks are given in Figures 4.14(b) and (c), together with typical values of impedances. A fault is assumed at A and it is desired to find the currents in branch OB due to the fault. In each network, the distribution factors are given for each branch, with the current in the fault branch taken as 1.0 p.u. From the diagram, the zero sequence distribution factor  $C_0$  in branch OB is 0.112 and the positive sequence factor  $C_1$  is 0.373. For an earth fault at A the phase currents in branch OB from Equation 4.35 are:

$$\begin{aligned} \bar{I}'_a &= (0.746 + 0.112)\bar{I}_0 \\ &= 0.858\bar{I}_0 \end{aligned}$$

and

$$\begin{aligned} \bar{I}'_b &= \bar{I}'_c = -(0.373 + 0.112)\bar{I}_0 \\ &= -0.261\bar{I}_0 \end{aligned}$$

By using network reduction methods and assuming that all impedances are reactive, it can be shown that  $\bar{Z}_1 = \bar{Z}_0 = j0.68$  ohms.

Therefore, from Equation 4.14, the current in fault

$$\text{branch } |I_a| = \frac{|V|}{0.68}$$

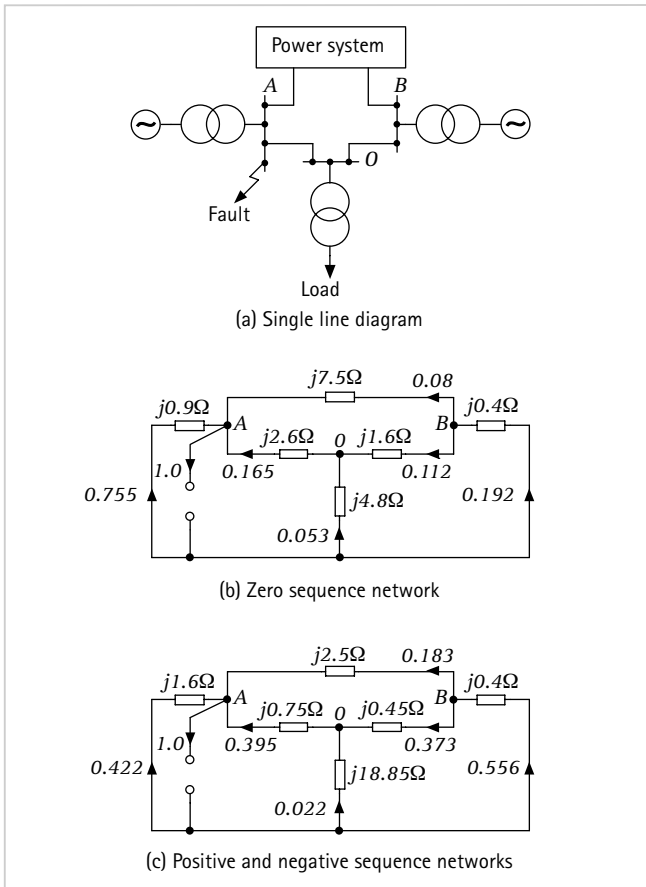
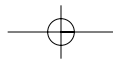


Figure 4.14: Typical power system

Assuming that  $|\bar{V}| = 63.5 \text{ volts}$ , then:

$$|I_0| = \frac{1}{3} |I_a| = \frac{63.5}{3 \times 0.68} = 31.2 \text{ A}$$

If  $\bar{V}$  is taken as the reference vector, then:

$$\begin{aligned} \bar{I}'_a &= 26.8 \angle -90^\circ \text{ A} \\ \bar{I}'_b &= \bar{I}'_c = 8.15 \angle -90^\circ \text{ A} \end{aligned}$$

The vector diagram for the above fault condition is shown in Figure 4.15.

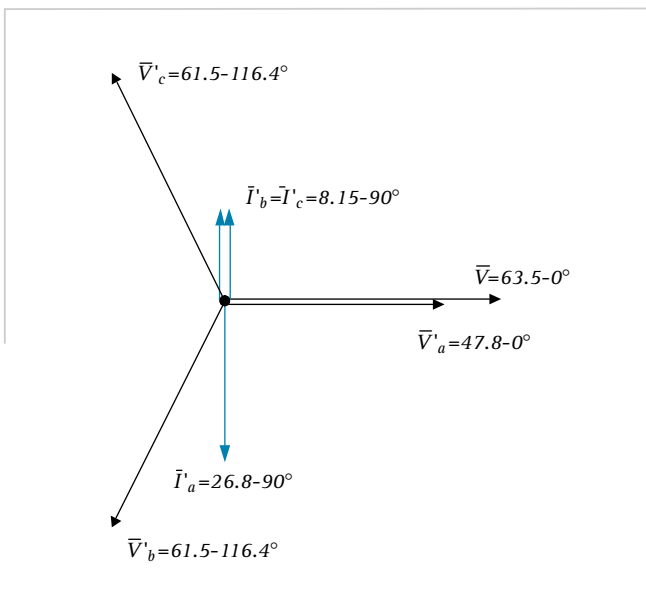


Figure 4.15: Vector diagram: Fault currents and voltages in branch OB due to P-E fault at bus A

### 4.5.2 Voltage Distribution

The voltage distribution in any branch of a network is determined from the sequence voltage distribution. As shown by Equations 4.4, 4.5 and 4.6 and the gradient diagrams, Figures 4.6(b) and 4.7(b), the positive sequence voltage is a minimum at the fault, whereas the zero and negative sequence voltages are a maximum. Thus, the sequence voltages in any part of the system may be given generally as:

$$\left. \begin{aligned} \bar{V}'_1 &= \bar{V} - \bar{I}_1 \left[ \bar{Z}_1 - \sum_1^n C_{1n} \Delta \bar{Z}_{1n} \right] \\ \bar{V}'_2 &= -\bar{I}_2 \left[ \bar{Z}_2 - \sum_1^n C_{2n} \Delta \bar{Z}_{2n} \right] \\ \bar{V}'_0 &= -\bar{I}_0 \left[ \bar{Z}_0 - \sum_1^n C_{0n} \Delta \bar{Z}_{0n} \right] \end{aligned} \right\} \dots \text{Equation 4.39}$$

Using the above equation, the fault voltages at bus B in the previous example can be found.

From the positive sequence distribution diagram Figure 4.8(c):

$$\bar{V}'_1 = \bar{V} - \bar{I}_1 \left[ \bar{Z}_1 - j \{ (0.395 \times 0.75) + (0.373 \times 0.45) \} \right]$$

$$\bar{V}'_2 = \bar{V} - \bar{I}_2 \left[ \bar{Z}_2 - j0.464 \right]$$

From the zero sequence distribution diagram Figure 4.8(b):

$$\begin{aligned} \bar{V}'_0 &= \bar{I}_0 \left[ \bar{Z}_0 - j \{ (0.165 \times 2.6) + (0.112 \times 1.6) \} \right] \\ &= \bar{I}_0 \left[ \bar{Z}_0 - j0.608 \right] \end{aligned}$$

For earth faults, at the fault  $\bar{I}_1 = \bar{I}_2 = \bar{I}_0 = j31.2 \text{ A}$ , when  $|\bar{V}| = 63.5 \text{ volts}$  and is taken as the reference vector. Further,  $\bar{Z}_1 = \bar{Z}_0 = j0.68 \text{ ohms}$ .

Hence:

$$\begin{aligned} \bar{V}'_1 &= 63.5 - (0.216 \times 31.2) \\ &= 56.76 \angle 0^\circ \text{ volts} \end{aligned}$$

$$\bar{V}'_2 = 6.74 \angle 180^\circ \text{ volts}$$

$$\bar{V}'_0 = 2.25 \angle 180^\circ \text{ volts}$$


and, using Equations 4.1:

$$\begin{aligned} \bar{V}_a &= \bar{V}'_1 + \bar{V}'_2 + \bar{V}'_0 \\ &= 56.76 - (6.74 + 2.25) \end{aligned}$$

$$\bar{V}'_a = 47.8 \angle 0^\circ$$

$$\begin{aligned} \bar{V}'_b &= a^2 \bar{V}'_1 + a \bar{V}'_2 + \bar{V}'_0 \\ &= 56.76a^2 - (6.74a + 2.25) \end{aligned}$$
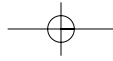
$$\bar{V}'_b = 61.5 \angle -116.4^\circ \text{ volts}$$



$$\begin{aligned} \bar{V}'_c &= a\bar{V}'_1 + a^2\bar{V}'_2 + \bar{V}'_0 \\ &= 56.75a - (6.74a^2 + 2.25) \\ \bar{V}'_c &= 61.5 \angle 116.4^\circ \text{ volts} \end{aligned}$$

These voltages are shown on the vector diagram, Figure 4.15.

#### 4.6 EFFECT OF SYSTEM EARTHING ON ZERO SEQUENCE QUANTITIES

It has been shown previously that zero sequence currents flow in the earth path during earth faults, and it follows that the nature of these currents will be influenced by the method of earthing. Because these quantities are unique in their association with earth faults they can be utilised in protection, provided their measurement and character are understood for all practical system conditions.

##### 4.6.1 Residual Current and Voltage

Residual currents and voltages depend for their existence on two factors:

- a. a system connection to earth at two or more points
- b. a potential difference between the earthed points resulting in a current flow in the earth paths

Under normal system operation there is a capacitance between the phases and between phase and earth; these capacitances may be regarded as being symmetrical and distributed uniformly through the system. So even when (a) above is satisfied, if the driving voltages are symmetrical the vector sum of the currents will equate to zero and no current will flow between any two earth points in the system. When a fault to earth occurs in a system an unbalance results in condition (b) being satisfied. From the definitions given above it follows that residual currents and voltages are the vector sum of phase currents and phase voltages respectively.

Hence:

$$\left. \begin{aligned} \bar{I}_R &= \bar{I}_a + \bar{I}_b + \bar{I}_c \\ \text{and} \\ \bar{V}_R &= \bar{V}_{ae} + \bar{V}_{be} + \bar{V}_{ce} \end{aligned} \right\} \dots \text{Equation 4.40}$$

Also, from Equations 4.2:

$$\left. \begin{aligned} \bar{I}_R &= 3\bar{I}_0 \\ \bar{V}_R &= 3\bar{V}_0 \end{aligned} \right\} \dots \text{Equation 4.41}$$

It should be further noted that:

$$\left. \begin{aligned} \bar{V}_{ae} &= \bar{V}_{an} + \bar{V}_{ne} \\ \bar{V}_{be} &= \bar{V}_{bn} + \bar{V}_{ne} \\ \bar{V}_{ce} &= \bar{V}_{cn} + \bar{V}_{ne} \end{aligned} \right\} \dots \text{Equation 4.42}$$

and since  $\bar{V}_{bn} = a^2 \bar{V}_{an}$ ,  $\bar{V}_{cn} = a \bar{V}_{an}$  then:

$$\bar{V}_R = 3\bar{V}_{ne} \dots \text{Equation 4.43}$$

where  $\bar{V}_{cn}$  - neutral displacement voltage.

Measurements of residual quantities are made using current and voltage transformer connections as shown in Figure 4.16. If relays are connected into the circuits in place of the ammeter and voltmeter, it follows that earth faults in the system can be detected.

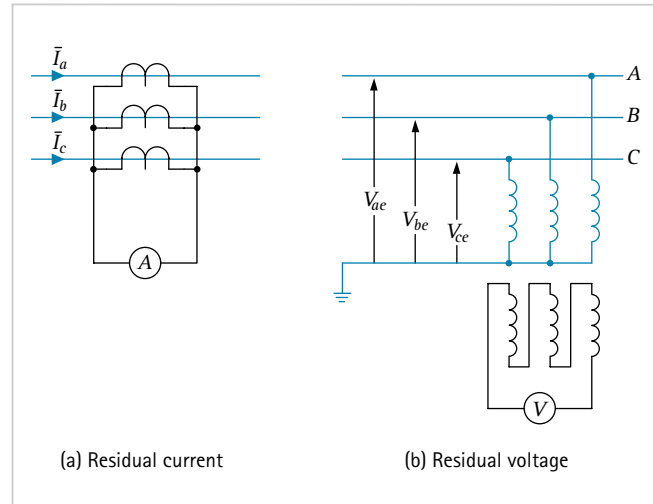


Figure 4.16: Measurement of residual quantities

##### 4.6.2 System $\bar{Z}_0 / \bar{Z}_1$ Ratio

The system  $\bar{Z}_0 / \bar{Z}_1$  ratio is defined as the ratio of zero sequence and positive sequence impedances viewed from the fault; it is a variable ratio, dependent upon the method of earthing, fault position and system operating arrangement.

When assessing the distribution of residual quantities through a system, it is convenient to use the fault point as the reference as it is the point of injection of unbalanced quantities into the system. The residual voltage is measured in relation to the normal phase-neutral system voltage and the residual current is compared with the three-phase fault current at the fault point. It can be shown [4.4/4.5] that the character of these quantities can be expressed in terms of the system  $\bar{Z}_0 / \bar{Z}_1$  ratio.

The positive sequence impedance of a system is mainly reactive, whereas the zero sequence impedance being affected by the method of earthing may contain both resistive and reactive components of comparable magnitude. Thus the express of the  $\bar{Z}_0 / \bar{Z}_1$  ratio approximates to:

$$\frac{\bar{Z}_0}{\bar{Z}_1} = \frac{\bar{X}_0}{\bar{X}_1} - j \frac{\bar{R}_0}{\bar{X}_1} \dots \text{Equation 4.44}$$

Expressing the residual current in terms of the three-phase current and  $\bar{Z}_0 / \bar{Z}_1$  ratio:

a. Single-phase-earth (A-E)

$$\bar{I}_R = \frac{3\bar{V}}{2\bar{Z}_1 + \bar{Z}_0} = \frac{3}{(2 + \bar{K})} \frac{\bar{V}}{\bar{Z}_1}$$

where  $\bar{K} = \bar{Z}_0 / \bar{Z}_1$

$$\bar{I}_{3\phi} = \frac{\bar{V}}{\bar{Z}_1}$$

Thus:

$$\frac{\bar{I}_R}{\bar{I}_{3\phi}} = \frac{3}{(2 + \bar{K})} \quad \dots \text{Equation 4.45}$$

b. Phase-phase-earth (B-C-E)

$$\bar{I}_R = 3\bar{I}_0 = -\frac{3\bar{Z}_1}{\bar{Z}_1 + \bar{Z}_0} \bar{I}_1$$

$$\bar{I}_1 = \frac{\bar{V}(\bar{Z}_1 + \bar{Z}_0)}{2\bar{Z}_1\bar{Z}_0 + \bar{Z}_1^2}$$

Hence:

$$\bar{I}_R = -\frac{3\bar{V}\bar{Z}_1}{2\bar{Z}_1\bar{Z}_0 + \bar{Z}_1^2} = -\frac{3}{(2\bar{K} + 1)} \frac{\bar{V}}{\bar{Z}_1}$$

Therefore:

$$\frac{\bar{I}_R}{\bar{I}_{3\phi}} = -\frac{3}{(2\bar{K} + 1)} \quad \dots \text{Equation 4.46}$$

Similarly, the residual voltages are found by multiplying Equations 4.45 and 4.46 by  $-\bar{K}\bar{V}$ .

a. Single-phase-earth (A-E)

$$\bar{V}_R = -\frac{3\bar{K}}{(2 + \bar{K})} \bar{V} \quad \dots \text{Equation 4.47}$$

b. Phase-phase-earth (B-C-E)

$$\bar{V}_R = \frac{3\bar{K}}{(2\bar{K} + 1)} \bar{V} \quad \dots \text{Equation 4.48}$$

The curves in Figure 4.17 illustrate the variation of the above residual quantities with the  $\bar{Z}_0 / \bar{Z}_1$  ratio. The residual current in any part of the system can be obtained by multiplying the current from the curve by the appropriate zero sequence distribution factor. Similarly, the residual voltage is calculated by subtracting from the voltage curve three times the zero sequence voltage drop between the measuring point in the system and the fault.

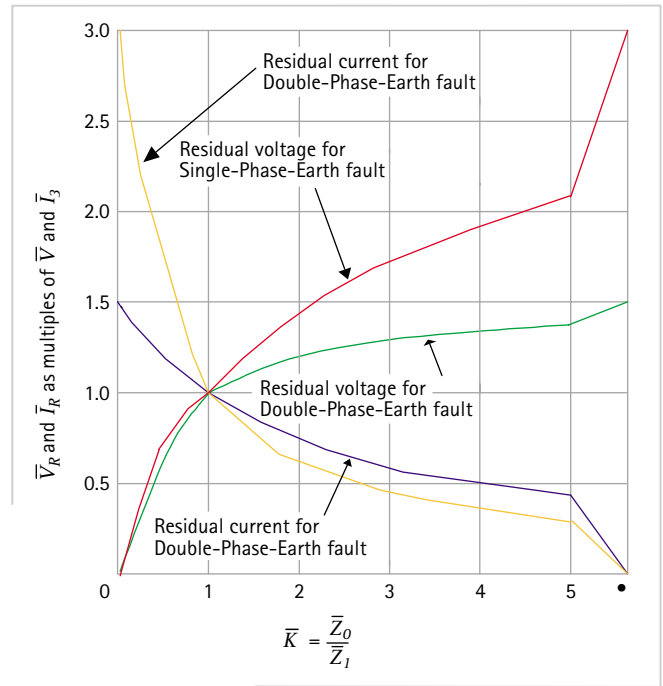


Figure 4.17: Variation of residual quantities at fault point

4.6.3 Variation of Residual Quantities

The variation of residual quantities in a system due to different earth arrangements can be most readily understood by using vector diagrams. Three examples have been chosen, namely solid fault-isolated neutral, solid fault-resistance neutral, and resistance fault-solid neutral. These are illustrated in Figures 4.18, 4.19 and 4.20 respectively.

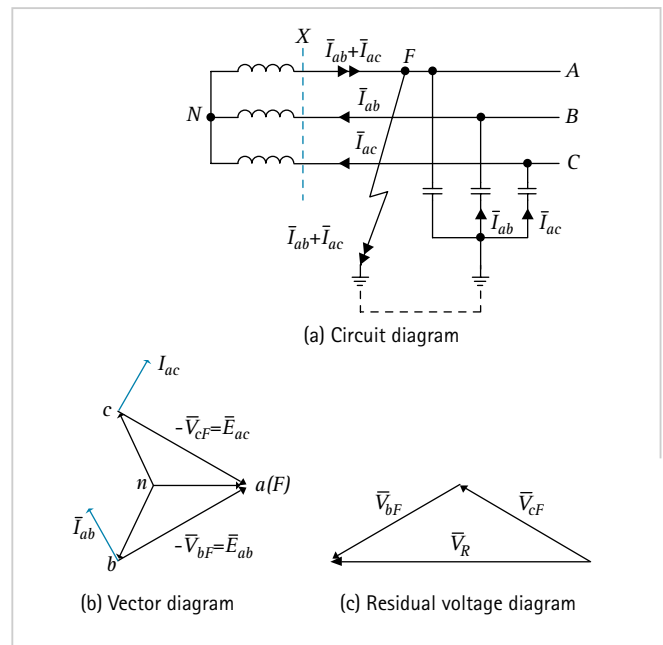


Figure 4.18: Solid fault-isolated neutral

### 4.6.3.1 Solid fault-isolated neutral

From Figure 4.18 it can be seen that the capacitance to earth of the faulted phase is short circuited by the fault and the resulting unbalance causes capacitance currents to flow into the fault, returning via sound phases through sound phase capacitances to earth.

At the fault point:

$$V_{aF} = 0$$

and

$$\begin{aligned} V_R &= \bar{V}_{bF} + \bar{V}_{cF} \\ &= -3\bar{E}_{an} \end{aligned}$$

At source:

$$\bar{V}_R = 3\bar{V}_{ne} = -3\bar{E}_{an}$$

since

$$\bar{E}_{an} + \bar{E}_{bn} + \bar{E}_{cn} = 0$$

Thus, with an isolated neutral system, the residual voltage is three times the normal phase-neutral voltage of the faulted phase and there is no variation between  $\bar{V}_R$  at source and  $\bar{V}_R$  at fault.

In practice, there is some leakage impedance between neutral and earth and a small residual current would be detected at X if a very sensitive relay were employed.

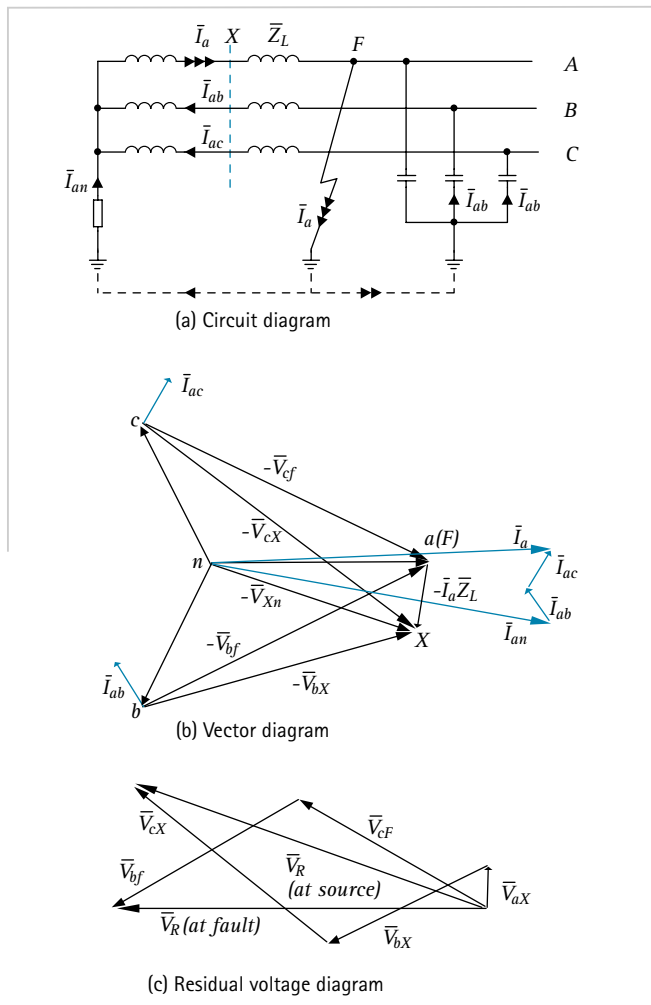


Figure 4.19: Solid fault-resistance neutral

### 4.6.3.2 Solid fault-resistance neutral

Figure 4.19 shows that the capacitance of the faulted phase is short-circuited by the fault and the neutral current combines with the sound phase capacitive currents to give  $\bar{I}_a$  in the faulted phase.

With a relay at X, residually connected as shown in Figure 4.16, the residual current will be  $\bar{I}_{an}$ , that is, the neutral earth loop current.

At the fault point:

$$\bar{V}_R = \bar{V}_{bF} + \bar{V}_{cF} \text{ since } \bar{V}_{Fc} = 0$$

At source:

$$\bar{V}_R = \bar{V}_{aX} + \bar{V}_{bX} + \bar{V}_{cX}$$

From the residual voltage diagram it is clear that there is little variation in the residual voltages at source and fault, as most residual voltage is dropped across the neutral resistor. The degree of variation in residual quantities is therefore dependent on the neutral resistor value.

### 4.6.3.3 Resistance fault-solid neutral

Capacitance can be neglected because, since the capacitance of the faulted phase is not short-circuited, the circulating capacitance currents will be negligible.

At the fault point:

$$\bar{V}_R = \bar{V}_{Fn} + \bar{V}_{bn} + \bar{V}_{cn}$$

At relaying point X:

$$\bar{V}_R = \bar{V}_{Xn} + \bar{V}_{bn} + \bar{V}_{cn}$$


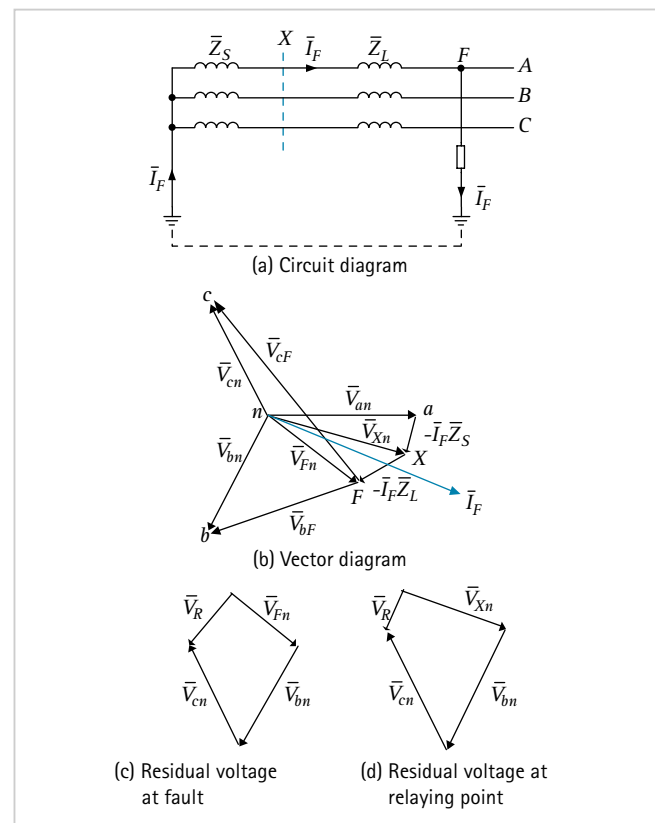


Figure 4.20: Resistance fault-solid neutral

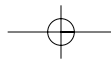

From the residual voltage diagrams shown in Figure 4.20, it is apparent that the residual voltage is greatest at the fault and reduces towards the source. If the fault resistance approaches zero, that is, the fault becomes solid, then  $\bar{V}_{Fn}$  approaches zero and the voltage drops in  $\bar{Z}_S$  and  $\bar{Z}_L$  become greater. The ultimate value of  $\bar{V}_{Fn}$  will depend on the effectiveness of the earthing, and this is a function of the system  $\bar{Z}_0 / \bar{Z}_1$  ratio.

#### 4.7 REFERENCES

- 4.1 *Circuit Analysis of A.C. Power Systems*, Volume I. Edith Clarke. John Wiley & Sons.
- 4.2 *Method of Symmetrical Co-ordinates Applied to the Solution of Polyphase Networks*. C.L. Fortescue. Trans. A.I.E.E., Vol. 37, Part II, 1918, pp 1027-40.
- 4.3 *Power System Analysis*. J.R. Mortlock and M.W. Humphrey Davies. Chapman and Hall.
- 4.4 *Neutral Groundings*. R Willheim and M. Waters, Elsevier.
- 4.5 *Fault Calculations*. F.H.W. Lackey, Oliver & Boyd.

